



D.Y. PATIL COLLEGE OF ENGINEERING & TECHNOLOGY
KASABA BAWADA KOLHAPUR-416006
(An Autonomous Institute)
S. Y. B. Tech-ETC (Semester-III)

Q. Paper Code:
22SYET202302

END SEMESTER EXAMINATION, OCT/NOV- 2021-22
COURSE NAME: Electronics Circuits Analysis and Design-I, COURSE CODE: 201ETL202

Day and Date: Thursday, 20/01/2022
Time: 11.00 am to 12.30 Pm

Seat No :
Max. Marks- 50

Instructions:

- i. All Questions are compulsory.
- ii. Figure to the right indicate full marks.
- iii. Use of non-programmable calculator is allowed.
- iv. Use of standard data sheet is allowed,

BT	CO's	Q. No.		Marks
		Q.1	Attempt the following	20
		a	Full wave rectifier uses diode with $R_f = 1\Omega$. Transformer is center tapped with output 10-0-10 Vrms and resistance of 5Ω for each section. Calculate. i) No load DC voltage ii) DC output at $I_L = 100\text{mA}$ & % Regulation. iii) Power conversion efficiency.	7
		b	For a zener shunt regulator if $V_z = 10\text{V}$, $R_s = 1\text{K}\Omega$, $R_L = 2\text{K}\Omega$ and input voltage varies from 20V to 40V, Find the maximum and minimum values of zener current.	7
		c	Write a note on "78 XX series and 79XX series".	6
		Q.2	Attempt the following	15
		a	Draw and explain RC high pass filter circuit, derive expression for output voltage of high pass filter. or With circuit and waveforms explain operation of combinational clipper.	7
		b	Draw and explain fixed bias circuit. Derive equation for I_B and V_{CE} .	8
		Q.3	Attempt the following	15
		a	Draw the drain characteristics of JFET, and explain all the regions. or Draw and explain the construction n-channel JFET.	7
		b	With circuit diagram explain the function of each component in single stage self-biased common emitter amplifier.	8
