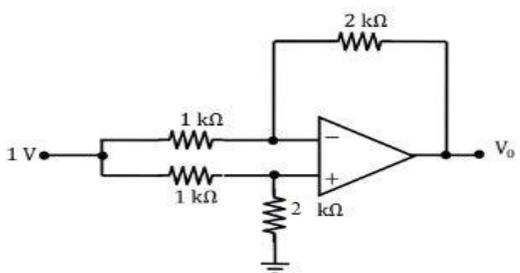
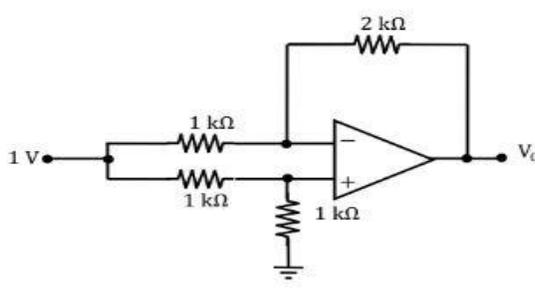


**Day and Date: Friday 24/06/2022**  
**Time: 9.30 am to 1.15 pm**


Seat No:
<b>Max. Marks- 100</b>

**Instructions:**

- i. Question No. 1 is compulsory.
- ii. Figure to the right indicate full marks.
- iii. Give suitable general Instructions


BT	CO's	Q. No.		Marks
		<b>Q.1</b>	<b>Attempt the following</b>	<b>40</b>
<b>L1</b>	<b>CO1</b>	<b>a</b>	i) Explain block diagram of Operational amplifier	<b>4</b>
<b>L2</b>			ii) Draw AC Equivalent circuit diagram of DIBO Differential amplifier & Derive the equation for Voltage gain $A_d$ .	<b>6</b>
<b>L1</b>	<b>CO1</b>	<b>b</b>	i) Draw & Describe high frequency equivalent circuits diagram of an op amp.	<b>3</b>
<b>L1</b>			ii) Draw & Describe voltage transfer characteristics of an op amp.	<b>3</b>
<b>L2</b>			iii) Define slew rate and describe effect of slew rate on sinusoidal signal.	<b>4</b>
<b>L2</b>	<b>CO2</b>	<b>c</b>	For the Op-amp circuit shown in the figure, $V_o$ is	<b>5</b>
<b>L2</b>			 <p>i)</p>	
			For the Op-amp circuit shown in the figure, $V_o$ is	<b>5</b>
			 <p>ii)</p>	

L1	CO3	d	i) Explain antilog amplifier using op amp. ii) For the circuit shown below, taking the opamp as ideal, the output voltage $V_{out}$ if $V_1, V_2$ and $V_3 = 1$ Volt each	5 5
L2				
		<b>Q.2</b>	<b>Attempt the following</b>	<b>20</b>
L1	CO4	a	Draw and explain First order Low pass Butterworth filter.	6
L1		b	Draw & Explain Band reject filter.	7
L3		c	Design a second order low pass filter at a high cutoff frequency of 1kHz . <b>OR</b> Design a second order High pass filter at a low cutoff frequency of 1kHz.	7
		<b>Q.3</b>	<b>Attempt the following</b>	<b>20</b>
L1	CO5	a	Draw & explain saw-tooth wave generator circuits.	6
L1		b	Describe RC Phase shift oscillator.	7
L1		c	With neat diagram explain Wien bridge oscillator. <b>OR</b> Draw square wave generator circuit using op amp. Derive equation for frequency of oscillation.	7
		<b>Q.4</b>	<b>Attempt the following</b>	<b>20</b>
L1	CO6	a	Draw & explain the block diagram of PLL	6
L1		b	Draw and explain the Monostable multivibrator using 555 Timer	7
L2		c	Find frequency of oscillation and duty cycle at output for given figure.	7

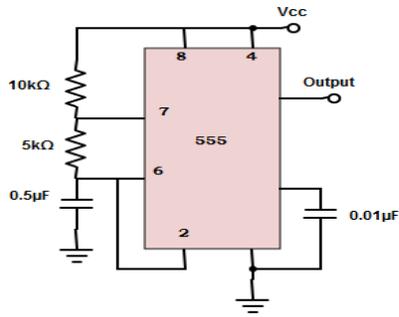

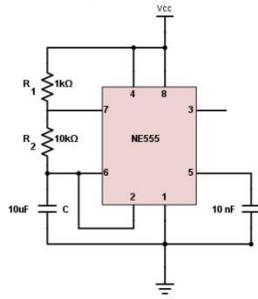**OR**

Find frequency of oscillation and duty cycle at output for given figure.



\*\*\*\*\*