

No Preview Available

Total No. of Question : [4]

Registration No. :

--	--	--	--	--	--	--	--	--	--

Programme Name : Bachelor of Electronics and Telecommunication Engineering
Regular S.Y.B.Tech.Sem.IV ESE May / June 2023
IV SEMESTER (2021 BATCH)
201ETL215- Linear Integrated circuit

Duration :

Marks : 50


Instructions :

(Q1) All questions are compulsory [20.0]

(1.1) Draw AC Equivalent circuit diagram of DIBO Differential amplifier & Derive the equation for Voltage gain A_d . [5.0]


CO :- CO1
Blooms Taxonomy :- Remember

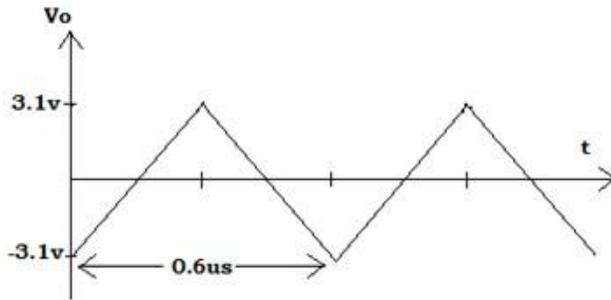(1.2) Find the slew rate of op-amp from the output waveform given below? [5.0]



CO :- CO1
Blooms Taxonomy :- Remember

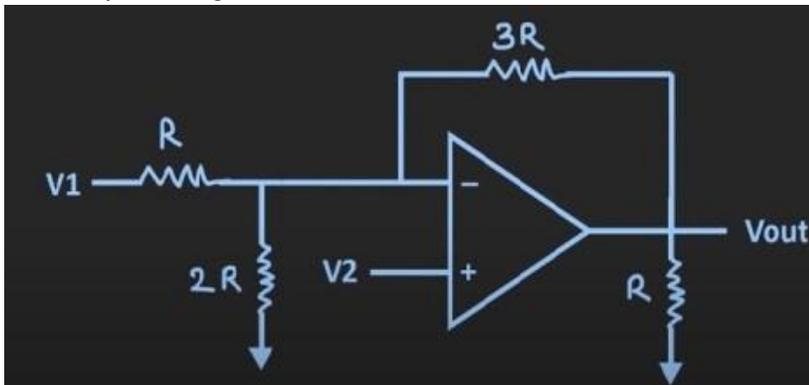
(1.3) Find output voltage when $V_1 = V_2 = 2V$ [5.0]



CO :- CO2
Blooms Taxonomy :- Apply

(1.4) Find the output voltage of following circuit

[5.0]

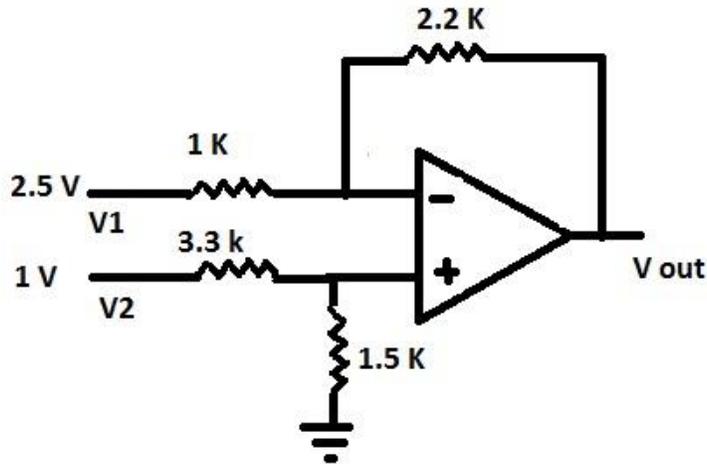

CO :- CO3

Blooms Taxonomy :- Understand

(Q2) Attempt the following

[10.0]

(2.1) Draw and explain second order high pass Butterworth filter.

[5.0]

CO :- CO4

Blooms Taxonomy :- Apply

(2.2) Design a second order low pass filter at a high cutoff frequency of 10kHz

[5.0]

CO :- CO4

Blooms Taxonomy :- Apply

OR [2.2 / 2.3]

(2.3) Design a second order High pass filter at a low cutoff frequency of 10kHz.

[5.0]

(Q3) Attempt the following

[10.0]

(3.1) Draw & explain saw-tooth wave generator circuits

[5.0]

CO :- CO5

Blooms Taxonomy :- Understand

(3.2) With neat diagram explain Wien bridge oscillator.

[5.0]

CO :- CO5

Blooms Taxonomy :- Understand

OR [3.2 / 3.3]

(3.3) Draw square wave generator circuit using op amp. Derive equation for frequency of oscillation.

[5.0]

CO :- CO5

Blooms Taxonomy :- Understand

(Q4)

Attempt the following

[10.0]

(4.1) Draw & Explain the block diagram of IC 8038

[5.0]

CO :- CO6

Blooms Taxonomy :- Apply

(4.2) Draw and explain the block diagram of 555 Timer

[5.0]

CO :- CO6

Blooms Taxonomy :- Apply

OR [4.2 / 4.3]

(4.3) Draw and explain the Monostable multivibrator using 555 Timer

[5.0]

CO :- CO6

Blooms Taxonomy :- Apply
