

Seat No.	
----------	--

S.E. (ETC) (Part - II) (Semester - IV) (Revised)

Examination, May -2019

LINEAR INTERGRATED CIRCUITS

Sub. Code : 63467

Day and Date : Thursday, 16 - 05 - 2019

Total Marks : 100

Time : 2.30 p.m. to 5.30 p.m.

- Instructions :**
- 1) All questions are compulsory.
 - 2) Figures to the right indicates full marks.

SECTION - I

Q1) Attempt any Two. [2×8=16]

- a) Draw AC equivalent circuit for DIBO-DA. Derive expression for R_i and R_o .
- b) Explain any four ideal and practical parameters of Op amp.
- c) With neat circuit diagram explain Instrumentation Amplifier using three op amp. Derive the expression for voltage gain for the same.

Q2) Attempt any two. [2×8=16]

- a) Discuss any two methods of frequency compensation used in op amp.
- b) Explain open loop and closed loop configuration of op amp.
- c) Draw and explain peak detector in details.

Q3) Write short notes on any three. [3×6=18]

- a) IC CA3140
- b) Thermal Drift
- c) Current mirror circuits
- d) Sample & Hold Circuits

P.T.O.

SECTION - II**Q4) Attempt any two.****[2×8=16]**

- a) With neat circuit diagram explain Wide Band Reject Filter with its frequency response.
- b) Design second order low pass butterworth filter with higher cut off frequency of 2KHz. Draw the design circuit diagram and sketch its frequency response. Assume $C = 0.01 \mu\text{f}$ and pass band gain = 1.586.
- c) With neat diagram explain Timer IC 555.

Q5) Attempt any two.**[2×8=16]**

- a) With neat circuit diagram explain Hartley and Colpitts oscillator using Op amp.
- b) Explain triangular wave generator with waveform.
- c) Explain with neat diagram and waveform use of IC 555 as monostable multivibrator.

Q6) Write short notes on any three.**[3×6=18]**

- a) IC OP 177 op amp
- b) IC 565 PLL
- c) RC phase shift oscillator
- d) Chebyshev filter

* * *

Seat No.	
----------	--

S.E. (ETC) (Semester - IV) Examination, May - 2019
ELECTROMAGNETICS ENGINEERING
Sub. Code : 63469

Day and Date : Wednesday, 22 - 05 - 2019

Total Marks : 100

Time : 2.30 p.m. to 5.30 p.m.

- Instructions :**
- 1) All Questions are compulsory.
 - 2) Neat diagrams must be drawn wherever necessary.
 - 3) Make suitable assumptions if necessary and state it clearly.

SECTION-I

Q1) Solve any two.

[2×8=16]

- a) A point charge $Q_1 = 2 \text{ mC}$ is located in free space at $P_1(-3, 7, 4)$ while $Q_2 = 5 \text{ mC}$ is at $P_2(2, 4, -1)$. Find F_2 & F_1 .
- b) A uniform line charge, $P_1 = 25 \text{ nC/m}$ lies on the line $X = -3, Z = 4$ in free space. Find E in Cartesian components at Origin
- c) Find the gradient of the function A given $A = \cosh xyz$.

Q2) Solve any two.

[2×8=16]

- a) Evaluate work done in bringing a charge of μC from origin to $P(2, -1, 4)$ through field $E = 2xyz \mathbf{a}_x + x^2z \mathbf{a}_y + x^2y \mathbf{a}_z$ (V/m) through the line path, straight line segments $(0, 0, 0)$ to $(2, 0, 0)$ to $(2, -1, 0)$ to $(2, -1, 4)$.
- b) Explain electric flux density D for point charge, line charge and surface charge.
- c) Evaluate Electric field intensity due to infinite line charge.

P.T.O.

Q3) Solve any three.

[3×6=18]

- What is polarization in dielectric?
- Explain the Cylindrical coordinate system.
- Write a note on boundary condition for dielectric - dielectric interface.
- Explain method of image for line charge.

SECTION-II

Q4) Solve any two.

[2×8=16]

- Derive Maxwell's equation in point form.
- State and explain Stoke's Theorem in Cartesian, Cylindrical and spherical co-ordinate system.
- A plane wave travelling in air is normally incident on a block of a paraffin with $\epsilon_r = 2.2$. Find Γ_R and Γ_T

Q5) Solve any two.

[2×8=16]

- A plane electromagnetic wave travelling in the +z direction in an unbounded lossless dielectric medium $\epsilon_r=3$, $\mu=1$ has peak electric intensity E of 6V/m Find
 - The velocity of wave
 - The intrinsic impedance of the wave
 - The peak value of the magnetic field intensity H.
- Estimate the incremental field dH_2 at point P_2 caused by a source at P_1 of $I_1 dL_1$
 $2\pi a_z - mt$, given $P_1(4,0,0)$ & $P_2(0,3,0)$
- Derive magnetic field intensity due to infinite long straight filament.

Q6) Solve any three.

[3×6=18]

- a) Derive transmission line equation.
- b) State and explain wavelength, velocity of propagation and group velocity.
- c) A lossless transmission line is 80 cm long and operates at a frequency of 600 MHz. The line parameters are $L = 0.25 \mu\text{H}/\text{m}$ and $C = 100 \text{ pF}/\text{m}$. Find the characteristic impedance, the phase constant and the phase velocity.
- d) An infinite long current filament is placed along z-axis. The magnetic field intensity at point P (3, 4, 0) is $I_0 (-0.8a_x + 0.6a_y) \text{ A/m}$. Find the current through the filament.



Seat No.	
----------	--

S.E. (ETC) (Part - II (Semester - III))

Examination, May - 2019

NETWORK ANALYSIS

Sub. Code : 63463

Day and Date : Tuesday, 07 - 05 - 2019

Total Marks : 100

Time : 10.00 a.m. to 1.00 p.m.


- Instructions :**
- 1) Figures to the right indicates full marks.
 - 2) All questions are compulsory.

SECTION - I

Q1) Solve any two.

[16]

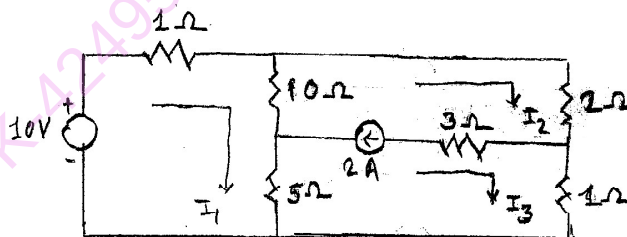- a) Determine current in 5Ω resistor for network shown in figure




- b) Write a note on tree, co-tree, twigs and links
c) Derive star-delta transformations.

Q2) Solve any two


[16]

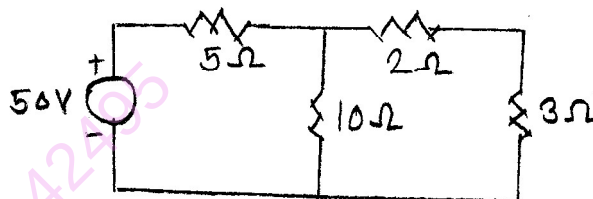- a) Use Thevenin's theorem to find the current in 3Ω resistor for the circuit shown in figure.



P.T.O.

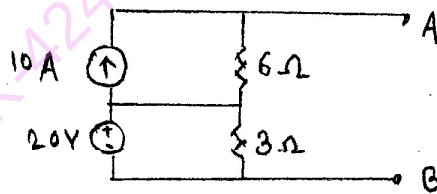- b) Replace the given network shown in figure by a single current source in parallel with a resistance.




- c) State and explain Millman's Theorem

Q3) Solve any two

[18]

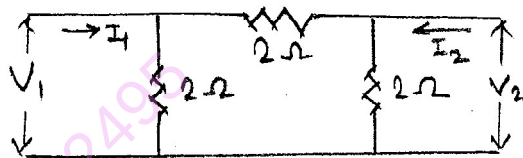- a) Derive series connection of two port network.
b) Find ABCD-Parameter for the following Circuit



- c) Explain short circuit admittance parameter.

SECTION - II

Q4) Solve any two

[18]

- a) Derive expression of resonance frequency for parallel resonance.
b) Show that $BW = (f_r/Q)$ for series RLC. Calculate f_0 , f_1 and f_2 for series RLC having 50Ω resistance, $0.2H$ inductance and $10\mu F$ capacitance with an applied voltage of $20V$.
c) Obtain the expression for frequency at which the maximum voltage across the inductor in series RLC.

Q5) Solve any two

- Design constant k type low pass filter (T and π -section) having design impedance of 600Ω and cutoff frequency is 1.5kHz .
- Derive expressions of Z_{OT} and $Z_{O\pi}$ for filters.
- Design m-derived high pass filter (T and π -section) having design impedance of 600Ω and cutoff frequencies are 10kHz and $m = 0.3$.

Q6) Solve any two

- Explain DC voltage response for RC circuit.
- Write short note on sinusoidal voltage response for RL circuit.
- For the following Fig. 6. C capacitor has initial voltage $V_C(-0) = 10\text{V}$ at the same instant current through inductor is zero, switch k is closed at $t = 0$. Find $V(t)$ across the inductor.

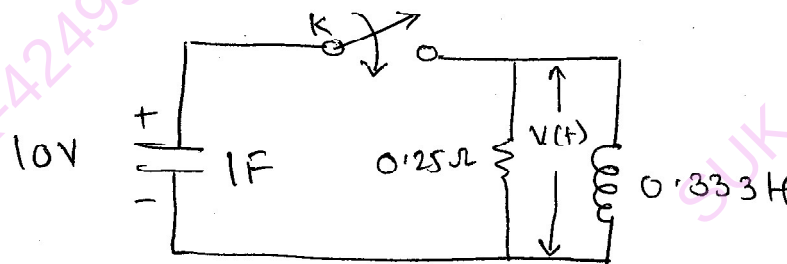


Fig. 6 C

x x x

Seat No.	
----------	--

**S.E. (Electronics and Telecommunication Engineering)
(Part - II) (Semester - III) Examination, April - 2019**

ENGINEERING MATHEMATICS - III

Sub. Code: 63460

Day and Date : Friday, 26 - 04 - 2019

Total Marks : 100

Time : 10.00 a.m. to 1.00 p.m.

- Instructions :**
- 1) All questions are compulsory.
 - 2) Figures to the right indicate full marks.
 - 3) Use of non-programmable calculator is allowed.

SECTION-I

Q1) Solve any three of the following.

- a) $(2D^2 + 5D - 3)y = \cos x$. [6]
- b) $(D^2 - 3D + 2)y = 5xe^x$. [6]
- c) $x^2 \frac{d^2y}{dx^2} + x \frac{dy}{dx} = x^2 + 5$. [6]
- d) $(2D^2 + 5D)y = 3x^2 + 2x + 1$ [6]

Q2) Solve any two of the following. [8]

- a) Find Fourier series for $f(x) = x^2$ in $(0, 2\pi)$ Hence deduce that $\frac{\pi^2}{3} = -\left\{ \frac{1}{1^2} + \frac{1}{2^2} + \frac{1}{3^2} + \dots \right\}$. [8]
- b) Find Fourier series for $f(x) = e^{-x}$ in the interval $(0, 2)$ [8]
- c) Obtain half range sine series for $f(x) = \cos x$ in the interval $(0, \pi)$. [8]

P.T.O.

Q3) Attempt any two of the following.

- a) Find Fourier Transform of $f(x) = \begin{cases} \frac{1}{2} & -1 \leq x \leq 1 \\ 0 & \text{otherwise} \end{cases}$ [8]
- b) Find Fourier Cosine Transform of $f(x) = e^{-x}$ and find $f(x)$ by using inverse Cosine Fourier transform. [8]
- c) Find finite Fourier Cosine Transform and its inverse of $f(x) = 2x$ in $0 < x < 4$. [8]

SECTION-II

Q4) Attempt any three of the following. [18]

- a) Find the Laplace transform of the periodic function $f(t) = \frac{kt}{T}, 0 < t < T, f(t+T) = f(t)$.
- b) Find the Laplace transform of $\sin \sqrt{t}$, hence find Laplace transform of $\frac{\cos \sqrt{t}}{2\sqrt{t}}$.
- c) Find the inverse Laplace transform of $\frac{s+4}{(s^2+4)s(s-1)}$.
- d) Using Laplace transform, solve $(D^2+2D+5)y = e^{-t} \sin t$ where $y(0) = 0$ $y'(0) = 1$.

Q5) Attempt any two of the following. [16]

- a) Find the Z-transform of $\sin(3k+5)$, $k \geq 0$.
- b) Find the Z-transform of the following functions
- i) $f(k) = 3(2^k) - 4(3^k)$, $k \geq 0$
 - ii) $f(k) = a^{|k|}$
- c) Find the inverse Z- transform of $\frac{2z^2 - 10z + 13}{(z-3)^2(z-2)}$, $2 < |z| < 3$.

Q6) Attempt any two of the following.

- a) A vector field $\vec{F}$ is given by

$\vec{F} = (y \sin z - \sin x)i + (x \sin z + 2yz)j + (xy \cos z + y^2)k$. Prove that it is irrotational and hence find its scalar potential.

- b) Find the constants a and b so that the surface $ax^2 - 2byz = (a+4)x$ will be orthogonal to the surface $4x^2y + z^3 = 4$ at $(1, -1, 2)$.

- c) Show that $\nabla \left[\frac{(\vec{a} \cdot \vec{r})}{r^n} \right] = \frac{\vec{a}}{r^n} - \frac{n(\vec{a} \cdot \vec{r})\vec{r}}{r^{n+2}}$, Where $\vec{r} = xi + yj + zk$ and $\vec{a} = a_1i + a_2j + a_3k$.



Seat No.	
----------	--

S.E. (E&TC) (Part - II) (Semester - III) (Revised)

Examination, May -2019

TRANSDUCERS & MEASUREMENT

Sub. Code : 63464

Day and Date : Thursday, 09 - 05 - 2019

Total Marks : 100

Time : 10.00 a.m. to 1.00 p.m.

- Instructions :**
- 1) All questions are compulsory.
 - 2) Figures to the right indicates full marks.

SECTION - I

Q1) Attempt any Two. [16]

- a) Define transducer. Explain the various factors for the selection of a transducer for a specific application.
- b) Explain the practical instrumentation amplifier used for temperature control in detail.
- c) Draw the block diagram of instrumentation system and explain each block in brief.

Q2) Attempt Any Two. [16]

- a) With the help of principle, construction and working explain the electromagnetic flowmeter.
- b) Explain with the help of neat diagram the motion transducer write the advantages and disadvantages.
- c) Explain phototransistor with the help of symbol. Construction, working and applications.

Q3) Write short notes on (any three): [18]

- a) Active band stop filter.
- b) Primary and secondary transducer.
- c) Active and passive instruments.
- d) Basic grounding methods.

P.T.O.

SECTION - II**Q4) Solve any two [16]**

- a) With block schematic & wave forms explain integrating type digital voltmeter.
- b) Explain different parts of Basic CRO with block schematic.
- c) Explain the static and Dynamic characteristics of an Instrument.

Q5) Solve any Two. [16]

- a) A sample of insulation was placed in arm AB of Schering bridge, when bridge was balanced at a frequency of 50Hz, then other arms of bridge were as follows
Arm BC – a non-inductive R of 100/ Ω
Arm CD – non-inductive R of 300/ Ω in parallel with capacitor of 0.5 μ F
Arm DA – a loss free capacitor of 100 pF.
Find capacitance, equivalent series resistance, & PF of insulation in test Arm AB.
- b) Explain measurement of frequency & phase using Lissajous pattern.
- c) Derive expression for frequency of a Wien Bridge.

Q6) Write short note on (Any three) [18]

- a) Logic Analyzer
- b) Maxwell - Wien bridge
- c) CRO - Probes
- d) Digital measurement of time.



Seat No.	
----------	--

**S.E. (Electronics & Telecommunication) (Semester - IV) (New)
(Revised) Examination, May - 2019**

DATA STRUCTURE

Sub. Code : 63468

Day and Date : Monday, 20 - 05 - 2019

Total Marks : 100

Time : 2.30 p.m. to 5.30 p.m.

- Instructions :**
- 1) All questions are compulsory.
 - 2) Figures to the right indicate full marks.
 - 3) Assume suitable data if necessary.

SECTION - I

Q1) Solve any two from three: [18]

- a) What is Binary Search method? Write C code for binary Search Algorithm.
- b) Describe with 'C' code deletion of nodes from linked list.
- c) Translate, by inspection, each infix expression to the corresponding postfix and prefix expression.
 - i) $((A + B) * D) / (E - F)$
 - ii) $A + B / C * (D + E / F - G) + H$

Q2) Solve any two from three: [16]

- a) What is time space trade off? Explain with example.
- b) Define stack and explain its representation using Linked list.
- c) What is Multidimensional array? Explain the representation of Two-dimensional array in memory?

Q3) Solve any two from three: [16]

- a) write 'C' code for
 - i) Removing element from Queue
 - ii) Inserting element into Queue
- b) Explain term Garbage collection? Also explain overflow & underflow situations.
- c) What is Linked list? Explain different types of Link list.

P.T.O.

SECTION - II

Q4) Solve any three.

[18]


- a) Represent the following algebraic expression in tree structure

$$E = [a + (b-c)] * [(d-e)/(f+g-h)]$$

- b) Construct a binary tree from the given order.

Postorder: HIDEBJFKGCA Inorder : HDIBEA FJCGK

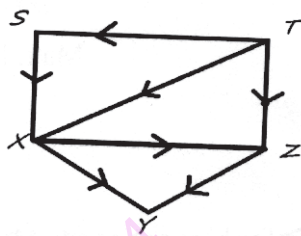- c) Explain deletion of a node from binary tree
- d) Consider graph G in the figure below, Suppose the nodes are stored in an array in a memory as follows X,Y,Z,S,T then



- i) Find the adjacency matrix A of G.
- ii) Find the path matrix P of G.
- iii) If G strongly connected?

Q5) Solve any three.

[16]

- a) Write an algorithm for preorder traversal.
- b) Write short note on "Threaded Trees"
- c) Write short note on topological sorting.
- d) Explain depth first algorithm.

Q6) Solve any two from three.

[16]

- a) Write an algorithm for post order traversal using stacks.
- b) Explain insertion in m-way search tree with proper example.
- c) Explain construction heap tree with example.



Seat No.	
-----------------	--

S.E. (ETC) (Part - II) (Semester - IV)
Examination, May - 2019
ANALOG COMMUNICATION SYSTEM
Sub. Code: 63470

Day and Date : Friday, 24- 05 - 2019

Total Marks : 100

Time : 2.30 p.m. to 5.30 p.m.

- Instructions :**
- 1) All questions are compulsory.
 - 2) Assume suitable data, if required.
 - 3) Figures to the right indicate full marks.

SECTION - I

Q1) Solve any three : **[3×6]**

- a) Draw and explain Trapezoidal patterns for AM.
- b) Draw and explain frequency spectrum and phase representation of AM wave.
- c) A carrier wave frequency of 10Mhz and peak value of 10V is applied and amplitude modulated by a 5Khz sine wave of amplitude 6V. Determine modulation index and sideband frequencies.
- d) Describe operation of phase shift method of SSB.

Q2) Solve any two : **[2×8]**

- a) Explain concept of angle modulation with respect to FM.
- b) Comment on pre-emphasis and de-emphasis used in FM.
- c) Write note on indirect method of FM generation.

Q3) Solve any Two: **[2×8]**

- a) Explain methods of tracking.
- b) Explain effect of AGC with characteristics
- c) Write note on image frequency and double spotting.

P.T.O.

SECTION - II**Q4) Solve any two :****[2×8]**

- a) Explain PLL-FM demodulator.
- b) Explain foster seeley discriminator.
- c) Explain in brief about noise figure, noise temperature, noise bandwidth, SNR.

Q5) Solve any two :**[2×8]**

- a) Explain shot noise, thermal noise, avalanche noise, burst noise.
- b) Write note on flat top sampling.
- c) Write note on classification of noise.

Q6) Solve any three**[3×6]**

- a) Explain PWM applications.
- b) Compare PAM with PWM.
- c) State and prove sampling theorem.
- d) Explain PCM transmitter.



Seat No.	
----------	--

S.E. (Electronics & Telecommunication) (Part - I)
(Semester - III) Examination, May - 2019
DIGITAL ELECTRONICS
Sub. Code : 63462

Day and Date : Saturday, 04 - 05 - 2019

Total Marks : 100

Time : 10.00 a.m. to 1.00 p.m.

- Instructions :
- 1) All questions are compulsory.
 - 2) Figures to the right indicate full marks.
 - 3) Assume appropriate data if needed.

Q1) Solve any two of the following. [16]

- a) Design and implement half adder with truth table.
- b) Design and implement one bit comparator.
- c) Give the specifications of digital IC's & explain propagation delay.

Q2) Solve any two of the following. [16]

- a) Design and implement 4 bit Binary to Gray code converter.
- b) Design 8:1 MUX using two 4:1 MUX.
- c) Design following logic function using 16:1MUX with truth table

$$F = \sum m(0,1,4,8,9,12,13,14).$$

Q3) Solve any two of the following. [18]

- a) Evaluate & minimize following expression using k-map

$$F(ABCD) = \sum m(0,1,4,5,6,7,9,11,15) + d(10,14).$$

- b) Design & implement 4 bit comparator using IC7485.
- c) Explain multiplexer IC 74151.

Q4) Attempt any three.**[18]**

- a) With suitable logic diagram and truth table explain SR flip flop with preset and clear inputs.
- b) Explain serial in serial out 4-bit shift register. Draw waveforms also.
- c) Write excitation table for SR, D and JK flip flop.
- d) Explain 3-bit ripple down counter with suitable state diagram and truth table.

Q5) Attempt any two.**[16]**

- a) Explain effect of clock skew and clock jitter on synchronous designs.
- b) Explain sequence detector with suitable example.
- c) Differentiate between Mealy & Moore machine.

Q6) Attempt any two.**[16]**

- a) Explain classification of memories in detail.
- b) Realize JK flip flop using SR flip flop.
- c) Explain Static and Dynamic RAM cell.



Seat No.	
-----------------	--

S.E. (E & TC) (Part - II) (Semester - IV)**Examination, May - 2019****ANALOG CIRCUITS - II****Sub. Code: 63466****Day and Date : Tuesday, 14- 05 - 2019****Total Marks : 100****Time : 2.30 p.m. to 5.30 p.m.**

- Instructions :**
- 1) All questions are compulsory.
 - 2) Assume suitable data, if required.
 - 3) Figures to the right indicate full marks.

SECTION - I (A)**Q1) Attempt any two :****[16]**

- a) Design two stage direct amplifier with transistor specification Q_1 and Q_2 .
 $h_{fe} = 100$, $I_{C(max)} = 100\text{mA}$, $V_{CE(max)} = 30\text{ V}$, $V_{O(p-p)} = 5\text{ V}$, $R_L = 10\text{k}\Omega$, $V_{CC} = 24\text{ V}$, $s = 5$
- b) Derive the parameter equations such as R_i , R_o , A_v and A_i for voltage series negative feedback.
- c) Design current series negative amplifier for following specifications : $V_{CC} = 12\text{V}$, $A_v = 30$, $S = 10$, use transistor BC147A.

Q2) Attempt any two :**[16]**

- a) Design two stage common emitter amplifier to provide the following specification.
 $V_{CC} = 10\text{V}$, $V_O = 3\text{V (rms)}$, $AVF \geq 100$, $R_S = 600\Omega$, $R_L = 1\text{ k}\Omega$,
 $f = 20\text{Hz}-20\text{ kHz}$, use transistor BC147B
- b) Design class AB push-pull amplifier for following specifications :
 $P_o = 400\text{mW}$, loud speaker impedance = 6Ω , $V_{CC} = 12\text{V}$
- c) Design class A push-pull amplifier for following specifications :
 $P_o = 500\text{mW}$, loud speaker impedance = 8Ω , $V_{CC} = 12\text{V}$

P.T.O.

Q3) Write note on any three [18]

- 3 point method of calculating harmonic distortion of power amplifier.
- Complementary symmetry power amplifier
- Types of negative feedback
- Classification of Power Amplifiers

SECTION - II (B)

Q4) Attempt any two : [16]

- Derive the expression for frequency of oscillation for Wein Bridge Oscillator.
- Design Hartley's Oscillator with following data $V_o = 6V$ (p-p), $F_o = 2MHz$, $S=9$. Transistor Data, $P_D = 0.2 W$, $V_{CE} (max) = 40V$, $h_{fe} = 110$, $h_{ie} = 2.7K\Omega$, $I_C (max.) = 0.1A$
- Design RC phase shift oscillator for following data, $F_o = 2.5KHz$, $I_C (sat.) = 4.5mA$, $h_{fe} = 50$, $h_{ie} = 4.5K\Omega$, $S=10$.

Q5) Attempt any two : [16]

- Design astable multivibrator for symmetric square wave with following data, Frequency = 500Hz, $V_o = 12V$, $h_{fe}(min) = 50$, $V_{BE}(sat.) = V_{CE}(sat.) = 0V$, $I_C (sat.) = 6mA$.
- Design power supply using LM 317 for following data $V_O = 8$ to $10V$ at $100mA$ current, and Input voltage in the range of $20V$ to $24V$.
- Design Monostable multivibrator for following data, $T_P = 2.5ms$, $V_{CC} = 10V$, $V_{BB} = -2V$, $V_{CE} (sat.) = 0.7V$, $I_C(sat.) = 5mA$, $C_1 = 0.3\mu F$, $h_{fe}(min) = 40$.

Q6) Write note on any three [18]

- IC 723.
- Barkhausen's criteria.
- Schmitt Trigger.
- Transistor switching parameters.

